

Total number of printed pages-4

3 (Sem-5/CBCS) PHY HE4

2021

(Held in 2022)

PHYSICS

(Honours Elective)

Paper : PHY-HE-5046

(Physics of Device and Instruments)

Full Marks : 60

Time : Three hours

**The figures in the margin indicate
full marks for the questions.**

1. Answer the following questions : $1 \times 7 = 7$

(a) Write the full form of MOSFET.

(b) Capacitor is a

(i) high-pass filter

(ii) low-pass filter

(iii) both high and low-pass filters

Contd.

- (c) What does the USB stand for ?
- (d) What is the difference between an astable multivibrator and a monostable multivibrator ?
- (i) The astable is free running
 - (ii) The astable needs to be clocked
 - (iii) The monostable is free running
- (e) What happens when the modulation index is greater than 1 ?
- (f) Mention *two* advantages of CMOS technology.
- (g) At critical frequency at which the response drop from the pass band is
- (i) -20 dB
 - (ii) -3 dB
 - (iii) 20 dB

2. Answer the following questions briefly :

$2 \times 4 = 8$

- (a) Give *two* differences between MOSFET and JFET.
- (b) Explain active and passive filter. Give an example of each.
- (c) What is RS232 communication ?

(d) Calculate the carrier frequency of an AM wave when its highest frequency component is 850 Hz and the bandwidth of the signal is 50 Hz.

3. Answer **any three** of the following questions : $5 \times 3 = 15$

(a) Give the circuit diagram and explain the working of a dc power supply using bridge rectifier and L-section filter.

(b) Explain the I-V characteristic of UJT. Explain its use as a relaxation oscillator.

(c) Give a short note on short circuit protection.

(d) What do you mean by USB standard? Give details of the USB 2.0.

(e) What is a tunnel diode? Explain its V-I characteristics.

4. Answer **any three** of the following questions :

(a) What is a sequential logic circuit? Draw the circuit diagram of a monostable multivibrator and explain its operation.

$2 + (2 + 6) = 10$

(b) Define low-pass filter and high-pass filter. Write the differences between them. $5+5=10$

(c) With a neat sketch, describe the construction of an n -channel JFET. Explain the principle of operation. $5+5=10$

Or

Explain with neat sketch the structure and working of p -channel enhancement type MOSFET. 10

(d) What is an IC circuit? What are the basic steps of IC fabrication? Explain etching and masking in case of IC fabrication. $5+5=10$

(e) Discuss the working of an exclusive-OR phase detector. Give the schematic diagram of PLL and explain its working. $5+5=10$

(f) What is amplitude modulation? Show that the amplitude modulation wave consists of a carrier and two sidebands. $3+7=10$

Or

Draw the circuit of a CE amplitude modulation and derive the expression for its output. 10