

- (b) What is a flip-flop? What are different types of flip-flops? Design a 3-bit counter using flip-flops.
- (c) Explain with a neat diagram, the working of a bridge rectifier.
- (d) What is shift register? What are the applications of shift register? Design a shift register using flip-flops.

5. Write short notes on **any two** of the following :
5×2=10

- (a) Universal logic gates
- (b) Capacitors
- (c) Multiplexer
- (d) Oscillators
-

Total number of printed pages-4

44 (2) BCA-HG-2016

2024

BASIC ELECTRONICS

Paper : BCA-HG-2016

Full Marks : 80

Time : Three hours

The figures in the margin indicate full marks for the questions.

1. Fill in the blanks : 1×8=8
- (a) The binary number 10101 is equivalent to decimal number ____.
- (b) The unit of resistances is ____.
- (c) The knee voltage for silicon *p-n* junction is ____ volt.
- (d) Diode is used as a ____.
- (e) The octal number system has a base of ____.

- (f) Oscillator employs _____ feedback.
- (g) The main function of a capacitor is _____.
- (h) A transistor has _____ terminals.

2. Answer the following questions in short :
2×6=12

- (a) Write *two* properties of semiconductor materials.
- (b) What do you mean by forward and reverse biasing of a *p-n* junction diode ?
- (c) Draw the symbol of NPN transistor and specify the terminals.
- (d) Write *two* applications of flip-flop.
- (e) Write the truth table of an exclusive OR (XOR) gate.
- (f) How will you obtain NOT gate from NAND gate ?

3. Answer **any four** questions from the following :
5×4=20

- (a) Draw and explain the V-I characteristic of a *p-n* junction diode.

- (b) Explain the basic laws of Boolean algebra.

- (c) What do you mean by minterm and maxterm ? Draw the logic diagram of the following :

$$Y = (A + BC)(B + \bar{C}A)$$

- (d) Design a S-R flip-flop using NAND gates. Write its truth table.

- (e) Mention some advantages of negative feedback.

- (f) Describe briefly different types of filters.

- (g) Explain briefly the working of a NPN transistor.

- (h) Simplify the Boolean function :

$$f(A,B,C,D) = \sum m(0,1,2,3,5,7,8,9,11,14)$$

4. Answer **any three** of the following questions :
10×3=30

- (a) What are different transistor configuration ? Explain CE configuration with neat diagram.